

Simulate the rectifier circuit shown in the diagram. The meters should be set to dc.


Use a sinusoidal supply of 10 V peak at a frequency of 50 Hz.

Suggested settings for the CRO are:


Time-base: 5 ms/div

Channel A: Vertical Deflection
5V/div

DC input

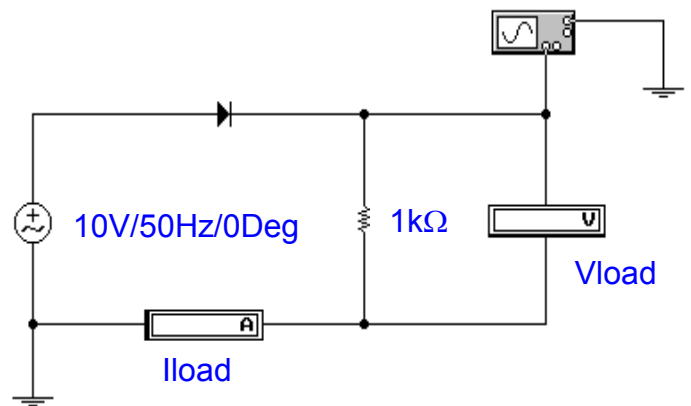

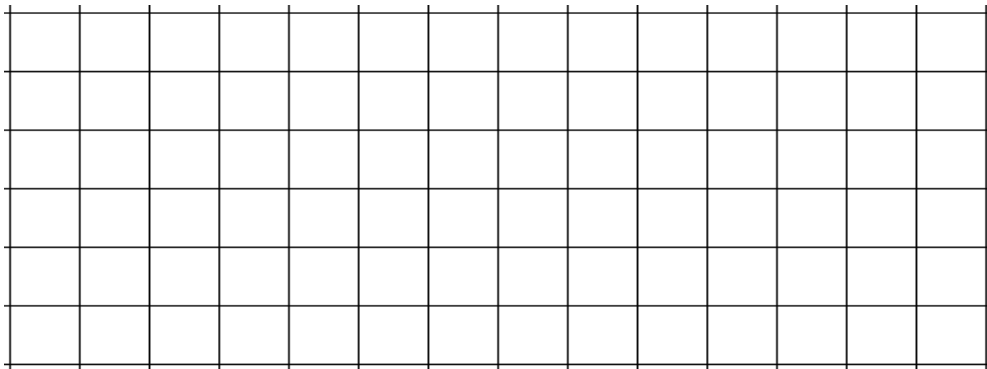Sketch the voltage waveform across the load resistor on the “oscilloscope screen” below. Label the axes and number the scales.



What is the name of this wave shape?

Record the following values

D.C. load voltage V_{load} (from the meter) = V

D.C. load current I_{load} (from the meter) = mA



Peak D.C. voltage (from the graph) = V

Why is V_{load} less than the peak voltage?

Calculate V_{load}/I_{load} Why is it this value?

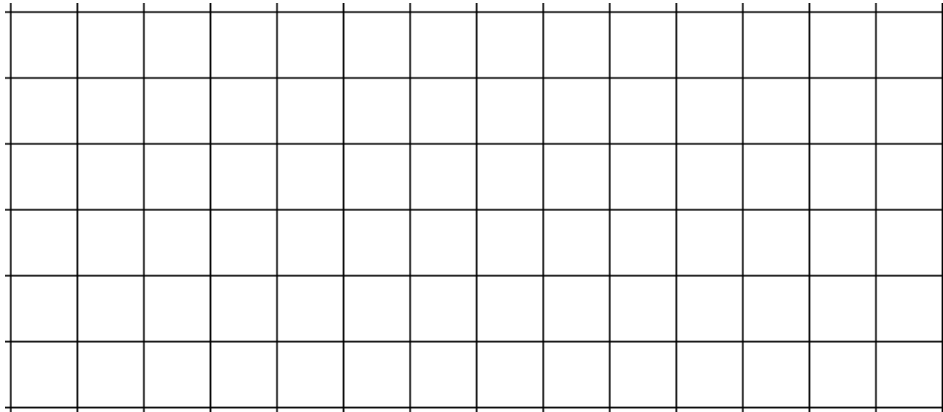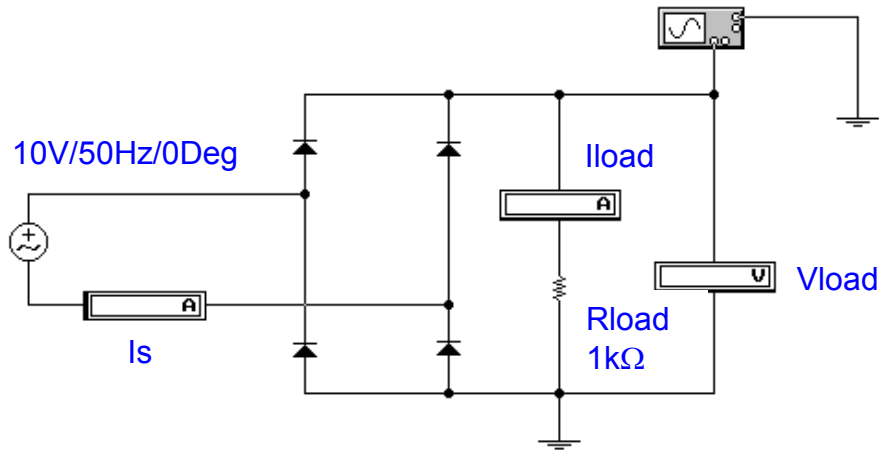Part 3. Full-wave Rectifier Circuit

Repeat the procedure of Part 2, but using the full-wave rectifier circuit shown below



Record the values of the d.c. load voltage and current (with the meters still set on dc).

$$V_{load} = \quad V \quad I_{load} = \quad mA$$

and calculate the ratio $V_{load}/I_{load} = \quad \Omega$.

What is this resistance?


Account for the difference in the two ammeter readings.

Why is V_{load} greater than in Part 2?

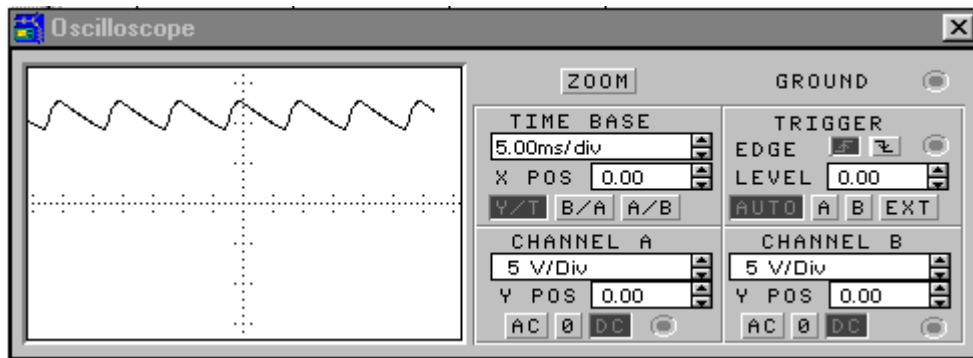Part 4. “Smoothing” The DC Output


Add a smoothing capacitor across the load resistor (try 22 μ F, 100 μ F, 1000 μ F) and see the ripple being reduced.

NB. if there is an error reported by EWB: Under Circuit, Analysis Options, alter Tolerance to 10%. (Reset this to 1% when you start Part 4).



Which capacitor gives the above trace?

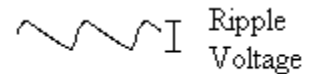Record the value of the “ripple voltage” for each capacitor




- 22 μ F
- 100 μ F
- 1000 μ F

Explain the effect of increasing the capacitor value.

What would happen if you increased the load resistor value?

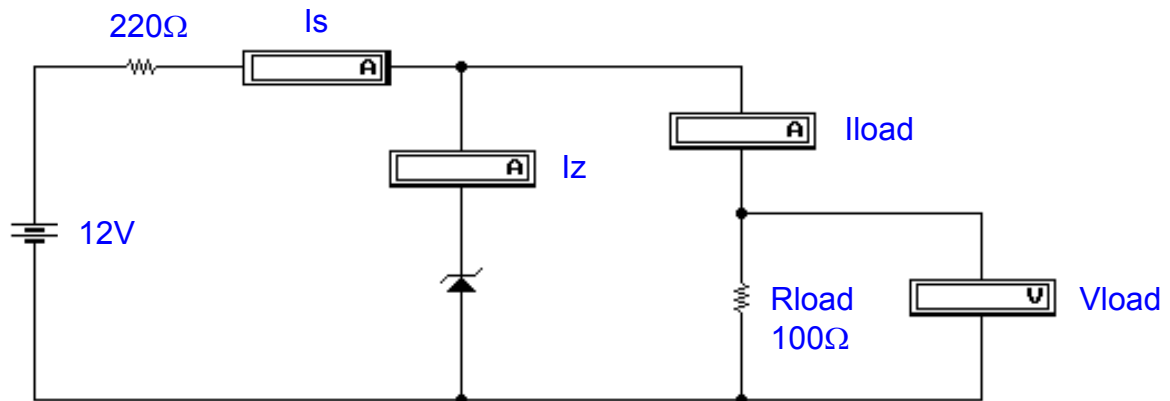Part 5. Zener Diode Voltage Stabiliser Circuit


Simulate the Zener diode circuit shown in the circuit below.



Record values of the load voltage, load current, Zener current and supply current for the range of load resistances shown in the table. Plot a graph of load voltage/load current.

Which axis is the vertical one? Hint: The voltage depends on the load current.

R_{load} (Ω)	V_{load} (V)	I_s (mA)	I_z (mA)	I_{load} (mA)
50 k				
5 k				
1 k				
500				
250				
175				
100				
50				

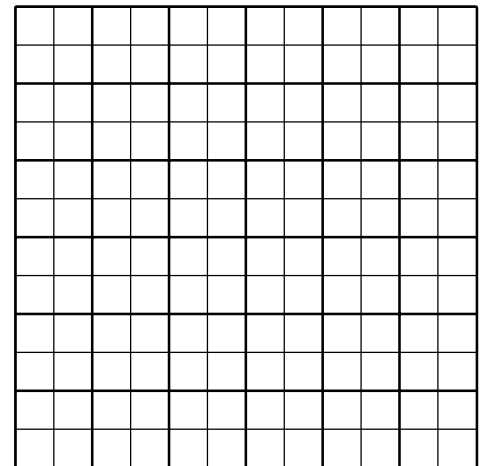

Highlight the zener diode symbol, and double click to inspect the Zener Diode models. Click on Edit. What is the zener voltage in the model?

Comment on the characteristic obtained, ie, what is the circuit supposed to do? Does the circuit work and if so, how well?