

DATE

COURSE/YEAR/GROUP

STUDENTS NAME

UNIVERSITY OF PLYMOUTH

Department of Communication and Electronic Engineering

EXPERIMENT FY2

RESPONSE OF A SERIES CONNECTED R-C CIRCUIT

OBJECTIVES

- (a) To investigate the response of a series connected R-C circuit to a d.c. input.
- (b) To investigate the concept of the TIME CONSTANT.

APPARATUS

Standard “Work Station” equipment available in Laboratory Room 304. Locktronics connection board and selection of resistors and capacitors.

INTRODUCTION

When a capacitor is charged from a d.c. supply through a resistor, the charging current is large at first, but gradually falls to zero as the capacitor voltage increases towards the supply voltage. The variation of the capacitor voltage with time has a characteristic EXPONENTIAL shape.

When a capacitor is discharged through a resistor, the capacitor voltage again varies exponentially, but in this case decreases with time.

These exponential variations have associated with them a “Time Constant”, which is a measure of how quickly the capacitor charges and discharges. This time constant is numerically equal to the product of the resistance and capacitance, i.e. time constant $\tau = RC$.

SECTION 1 CAPACITOR CHARGING

Connect the circuit as shown in Fig. 1. Using the d.c. power supply to produce the 12 V input voltage. NB Check the voltage with the Voltmeter. To permit visual reading of the capacitor voltage variation, the values of resistance and capacitance must be relatively large. **NOTE: the polarity of the capacitor.** With the SWITCH OPEN, discharge the capacitor by shorting it with a 1k Ω resistor. Close the switch and take readings of time as the capacitor voltage increases.


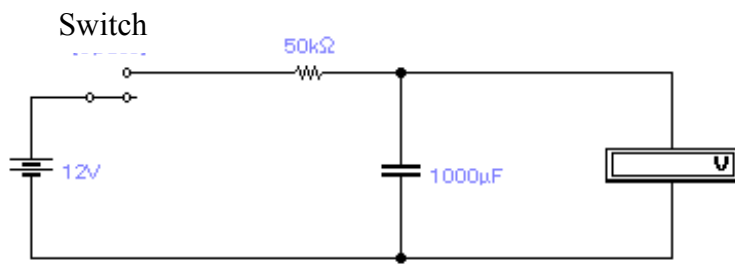


Fig. 1

Capacitor Voltage V	Time s
1	
2	
3	
4	
6	
8	
10	
11.5	

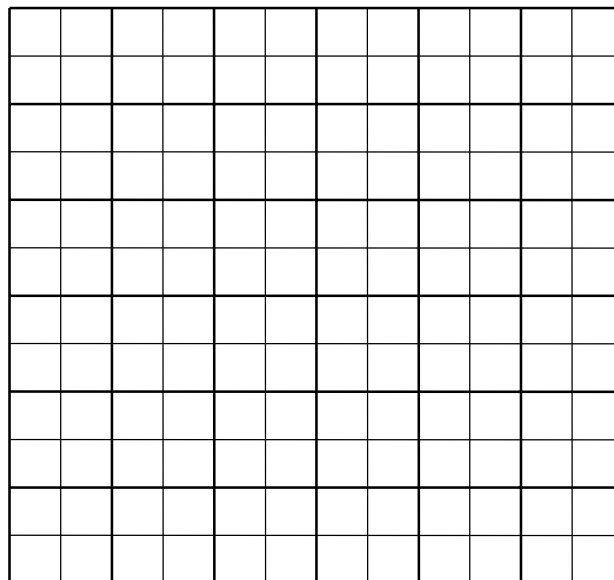Plot the capacitor voltage against time of the graph below.



Determine the TIME CONSTANT using the following methods:

(i) Calculate the time constant using $\tau = RC$ $\tau = \dots\dots\dots$ s

(ii) Estimate the time constant by determining the time taken for the capacitor voltage to reach 0.632 times the supply voltage, i.e. $0.632 \times 12V = 7.58V$ in this case.
 Note: this is approximately 2/3 of the supply voltage.
 $\tau = \dots\dots\dots$ s

(iii) Estimate the time constant by drawing a tangent to the capacitor voltage curve at time $\tau = 0$, i.e. a line denoting the initial slope of the curve, and find the time at which this line passes through the supply voltage level.
 $\tau = \dots\dots\dots$ s

Compare the values obtained for the time constant using the three methods.

Using the above graph, determine time constant by:

- (i) estimating the time taken for the voltage to reach 0.368 times the supply voltage (i.e. approximately 1/3 of the supply voltage).

Time Constant $\tau = \dots\dots\dots$ s

- (ii) drawing a tangent to the curve at $\tau = 0$ and projecting down to find the time at which the tangent passes through the zero voltage position.

Time Constant $\tau = \dots\dots\dots$ s

Using the plotted variation of capacitor voltage, after how many time constants may the capacitor voltage be assumed to have reached steady-state (i.e. within 5%)?

Number of time constants = $\dots\dots\dots$

SECTION 4: RESPONSE OF R-C SERIES CIRCUIT TO SQUARE WAVE INPUT

Connect the circuit as in Fig. 1 but using $C = 0.1 \mu\text{F}$ and $R = 1\text{k}\Omega$. Replace the P.S.U. with the Function Generator and set the output to give a 5 V peak-to-peak SQUARE WAVE at 1 kHz.

Display the capacitor voltage on the oscilloscope and record the waveform using the graph on the next page.

Repeat the procedure for values of the resistance $R = 2.5 \text{ k}\Omega$ and $R = 5 \text{ k}\Omega$

Calculations:

Square wave input is at 1 kHz, therefore period of waveform = $\dots\dots\dots$ s.

Hence, time for one half period of the waveform is $\dots\dots\dots$ s.

Calculate the Time Constant for the circuit using $\tau = RC$.

When $R = 1\text{k}\Omega$ Time Constant $\tau = \dots\dots\dots$ s


$R = 2.5\text{k}\Omega$ Time Constant $\tau = \dots\dots\dots$ s

$R = 5\text{k}\Omega$ Time Constant $\tau = \dots\dots\dots$ s


Discussions:

Use the values calculated above to explain the capacitor voltage waveforms recorded.


$R = 1\text{k}\Omega$

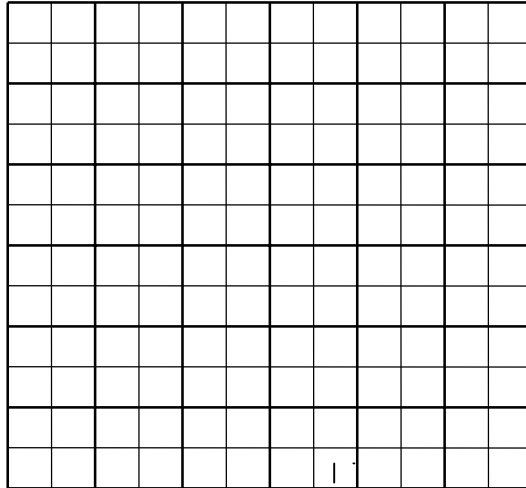

$R = 2.5\text{k}\Omega$


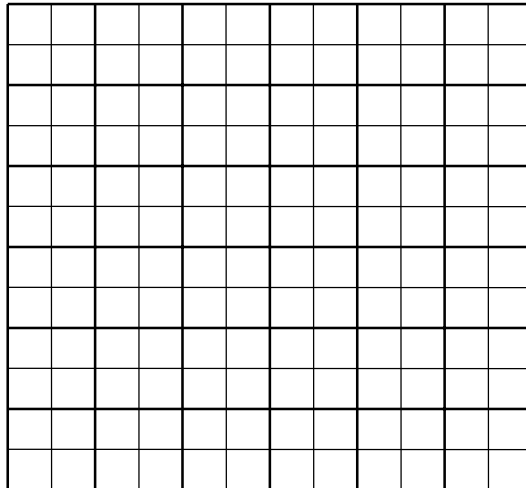


$R = 5\text{k}\Omega$

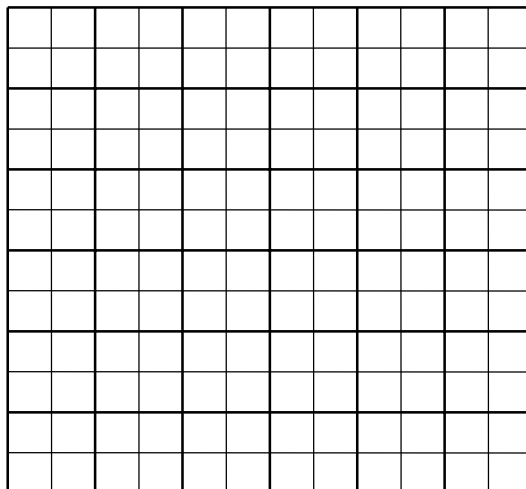

Response of a Series Connected R-C Circuit
(supplement)

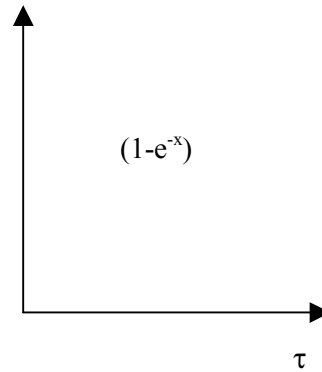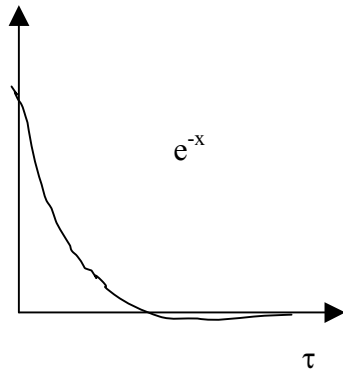Graphs of the following forms have the following equations:-



E.g. for charging $V_R = V_S e^{-\frac{t}{RC}}$
 $I_C = I_{\max} e^{-\frac{t}{RC}}$

$V_C = V_S (1 - e^{-\frac{t}{RC}})$

where $V_S = 12 \text{ V}$, $I_{\max} = \frac{V_S}{R}$

Prove these equations are correct by calculating values and then comparing with your graph.

(N.B. Check your $V_S = 12 \text{ V}$, or use the actual voltage in the calculations).

t/seconds =	60	100	180
V_C Calc			
V_C Graph			
% difference			


General Technique

If we have a series of results and want to find the equation, we take logs (ln) to get a straight line graph (i.e. of the form $y = mx + c$) and then calculate m (gradient) and C (the y axis intercept).

Example for Discharge results:

Add another column and then plot $\ln(V_C)$ against τ .

T	V_C	$\ln(V_C)$

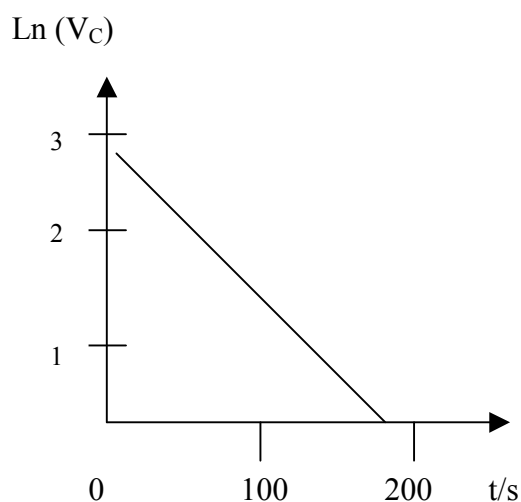

Slope of graph = _____

Theory

$$V_C = V_S e^{-\frac{t}{RC}}$$

$$\ln(V_C) = \ln(V_S e^{-\frac{t}{RC}})$$

$$\ln(V_C) = \ln(V_S) - \frac{t}{RC} \quad (\text{as } \ln(e^Z) = Z)$$

Compare with $y = c + mx$ (general form of a straight line equation) i.e. $m = -\frac{1}{RC}$
(as $y = \ln(V_S)$ and $x = \tau$)

$$\therefore \text{slope of graph} = -\frac{1}{RC} ; RC = -\frac{1}{\text{Slope}} = \underline{\hspace{2cm}}$$

How well does this compare with the component RC ? _____